

Lab Session 5

ALU and Register Files

Advisor: Lih-Yih Chiou

Speaker: Patty


Date: 03/23/2016

Outline

- Introduction
- Lab A : Arithmetic Logic Unit
- Lab B : Register File
- Lab C : Serial-In Parallel-Out Register File
- Lab D : Register File + ALU
- Lab5 Homework
- Copy Reference code

Introduction


Single-Cycle CPU

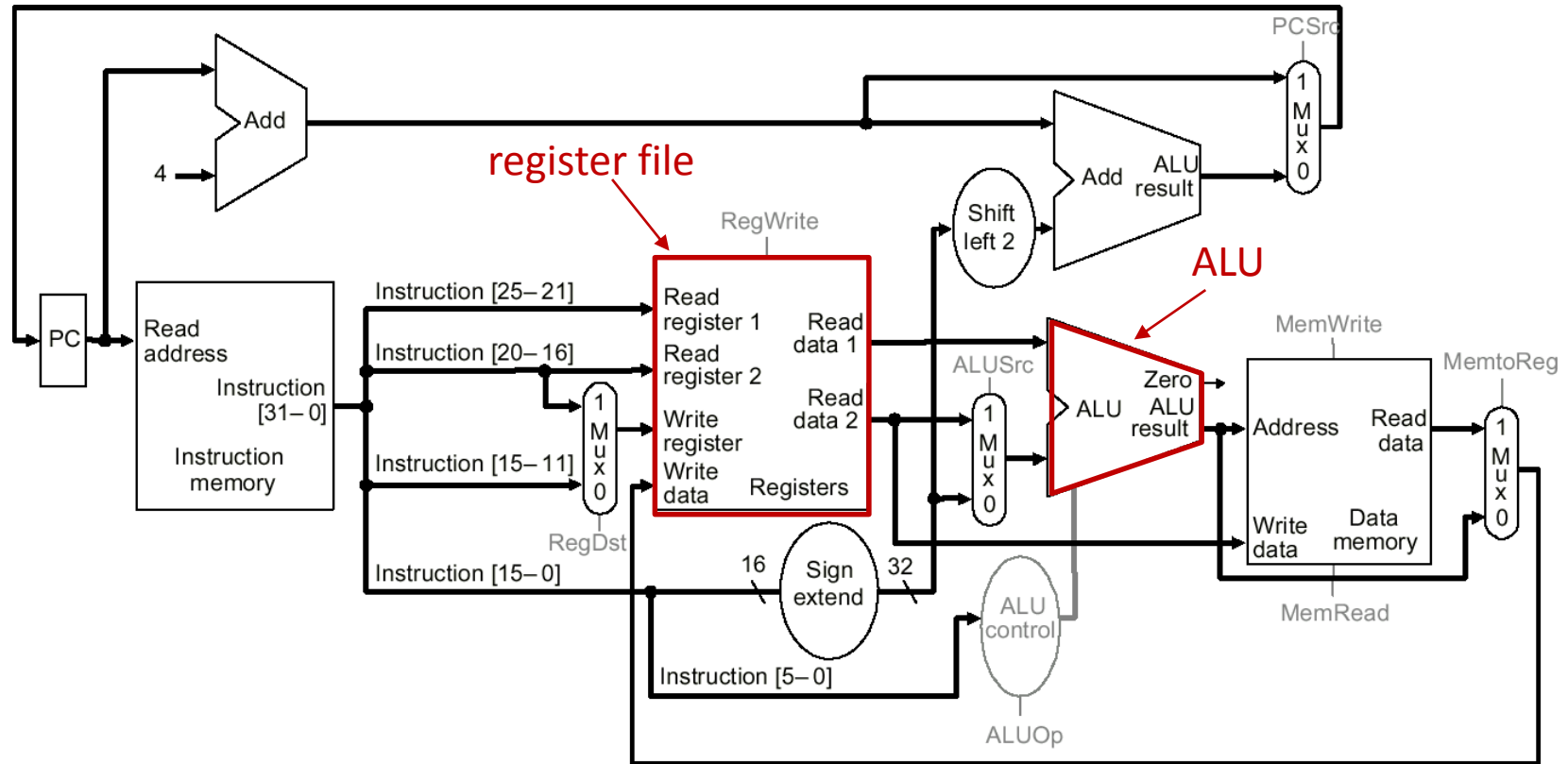

Computer Organization and Design. THE HARDWARE/SOFTWARE INTERFACE. David A. Patterson, John L. Hennessy

Lab A : Arithmetic Logic Unit

 - A digital electronic circuit that performs arithmetic and bitwise logical operations on integer binary numbers
- A fundamental building block of the CPU.





Lab A : Arithmetic Logic Unit

Signal	Type	Bits	Description
alu_enable	input	1	0→close 1→open
alu_op	input	4	Operation code select which operation to be executed
src1	input	32	ALU source 1
src2	input	32	ALU source 2
alu_out	output	32	ALU result
alu_overflow	output	1	0→no overflow 1→overflow

NOTE :

Definition of overflow : the result is greater than which a given register can store or represent.

  ADD pos + pos = neg
 ADD neg + neg = pos
 SUB pos - neg = neg
 SUB neg - pos = pos



Lab A : Arithmetic Logic Unit

Category	alu_op	Operation	Description
Arithmetic	0000	ADD	alu_out = src1 + src2
	0001	SUB	alu_out = src1 - src2
Logical	0010	AND	alu_out = src1 & src2
	0011	OR	alu_out = src1 src2
	0100	XOR	alu_out = src1 ^ src2
	0101	NOR	alu_out = ~(src1 src2)
Barrel shifter	0110	SRL	alu_out = src1 >> src2
	0111	ROTR	alu_out = src1 rotate right by "src2 bits"

NOTE :

Difference between **shift** and **rotate** :

SRL 8'b0000_1**111** >> 8'b0000_0011 = 8'b**0000**_0001

ROTR 8'b0000_1**111** rotate right 8'b0000_0011 = 8'b**1110**_0001

Lab A : Reference Code (1/2)

```

1  `timescale 1ns/10ps
2
3  // ----- define ----- //
4
5  `define DataSize    32
6  `define ALUopSize   4
7  //define ALUop
8  `define ADDop       4'b0000
9  `define SUBop       4'b0001
10 `define ANDop        4'b0010
11 `define ORop         4'b0011
12 `define XORop        4'b0100
13 `define NORop        4'b0101
14 `define SRLop        4'b0110
15 `define ROTRop       4'b0111
16
17 module ALU (alu_enable, alu_op, src1, src2, alu_out, alu_overflow);
18
19 // ----- input ----- //
20 input          alu_enable;
21 input  [`ALUopSize-1:0] alu_op;
22 input  [`DataSize-1:0]  src1;
23 input  [`DataSize-1:0]  src2;
24
25 // ----- output ----- //
26 output  [`DataSize-1:0] alu_out;
27 output          alu_overflow;
28
29 // ----- reg ----- //
30 reg  [`DataSize-1:0] alu_out;
31 reg          alu_overflow;
32 reg  [63:0] temp;

```

Increase modifiability
and readability

Lab A : Reference Code (1/2)

If there is any change on the RHS of "=",
the always block will be executed

readability

```

33
34 always@(*)begin
35     alu_overflow = 1'b0;
36     if(alu_enable)begin
37         case(alu_op)
38             ADDop : begin
39                 alu_out = src1 + src2;
40                 if((src1[31]==0 && src2[31]==0 && alu_out[31]==1)||
41                    (src1[31]==1 && src2[31]==1 && alu_out[31]==0))
42                     alu_overflow = 1'b1;
43                 else
44                     alu_overflow = 1'b0;
45                 end
46             `SUBop : begin
47                 alu_out = src1 - src2;
48                 if((src1[31]==0 && src2[31]==1 && alu_out[31]==1)||
49                    (src1[31]==1 && src2[31]==0 && alu_out[31]==0))
50                     alu_overflow = 1'b1;
51                 else
52                     alu_overflow = 1'b0;
53                 end
54             `ANDop : alu_out = src1 & src2;
55             `ORop  : alu_out = src1 | src2;
56             `XORop : alu_out = src1 ^ src2;
57             `NORop : alu_out = ~(src1 | src2);
58             `SRLop : alu_out = src1 >> src2;
59             `ROTRop : begin
60                 temp = {src1,src1};
61                 temp = temp >> src2;
62                 alu_out = temp[31:0];
63             end
64             default : alu_out = 32'b0;
65         endcase
66     end
67 else
68     alu_out = 32'b0;
69 end
70 endmodule

```

case

full case

Lab B : Register File

□ D Latch


 


Fig. D latch with enable

E	D	Q	Q_{next}	Q'_{next}
0	x	0	0	1
0	x	1	1	0
1	0	x	0	1
1	1	x	1	0

Lab B : Register File

□ D flip-flop

 

clk	D	Q	Q_{next}	Q'_{next}
0	x	0	0	1
0	x	1	1	0
1	x	0	0	1
1	x	1	1	0
\uparrow	0	x	0	1
\uparrow	1	x	1	0

Fig. Positive-edge-triggered D flip-flop

Lab B : Register File


□ The main difference between latch and flip-flop

➔ Latch

- ◆ Outputs are constantly affected by the inputs as long as the enable signal is asserted.

➔ Flip-Flop

 - ◆ Outputs change only at the rising edge of the clock signal.



Lab B : Register File

- ❑ Register file is an **array** of processor registers in a CPU.
 - ➔ A 32 X 32 register file means it has 32 registers and each of them is 32 bits.
- ❑ Components
 - ➔ n to 1 Decoder
 - ➔ Array
 - ➔ m to n Multiplexer
- ❑ Multiple output ports allow us to read several data in one cycle.

 


Fig. Memory Hierarchy

Lab B : Register File

How does it work ?

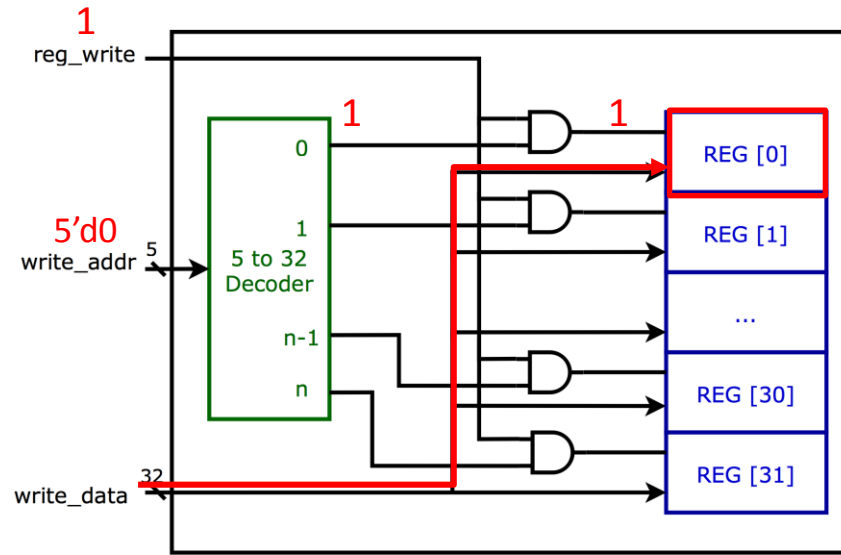


Fig. Write data into register file


 


Fig. Read data from register file

Lab B : Register File


Port List

Signal	Type	Bits	Description
clk	input	1	clock
rst	input	1	reset
reg_enable	input	1	0 → off 1 → on
reg_write	input	1	0 → read 1 → write
src1_addr	input	5	source1 address
src2_addr	input	5	source2 address
write_addr	input	5	write address
write_data	input	32	write data
src1	output	32	read data source1
src2	output	32	read data source2

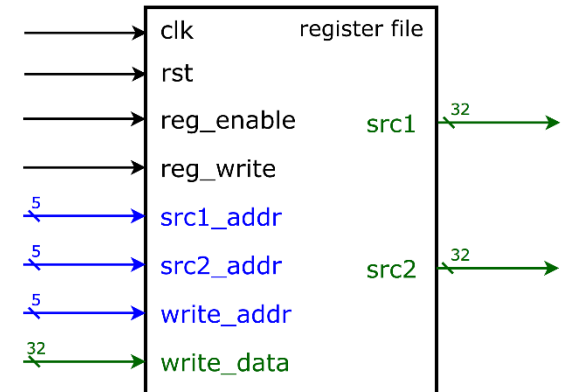

Lab B : Register File


□ How does it write?

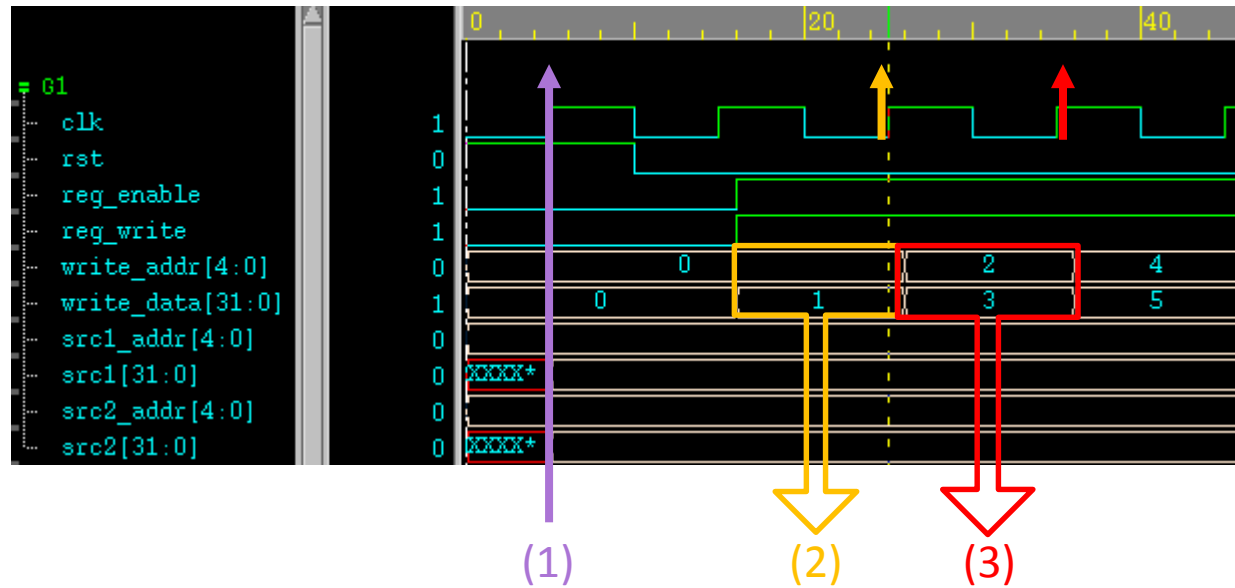

- (1) clock positive edge↑, reset signal is set to 1, all registers are reset to zero
- (2) clock positive edge↑, register file is enable and in write mode
→ `32'd1` is written into `REG[0]`
- (3) clock positive edge↑, register file is enable and in write mode
→ `32'd3` is written into `REG[2]`

Lab B : Register File

□ How does it read?

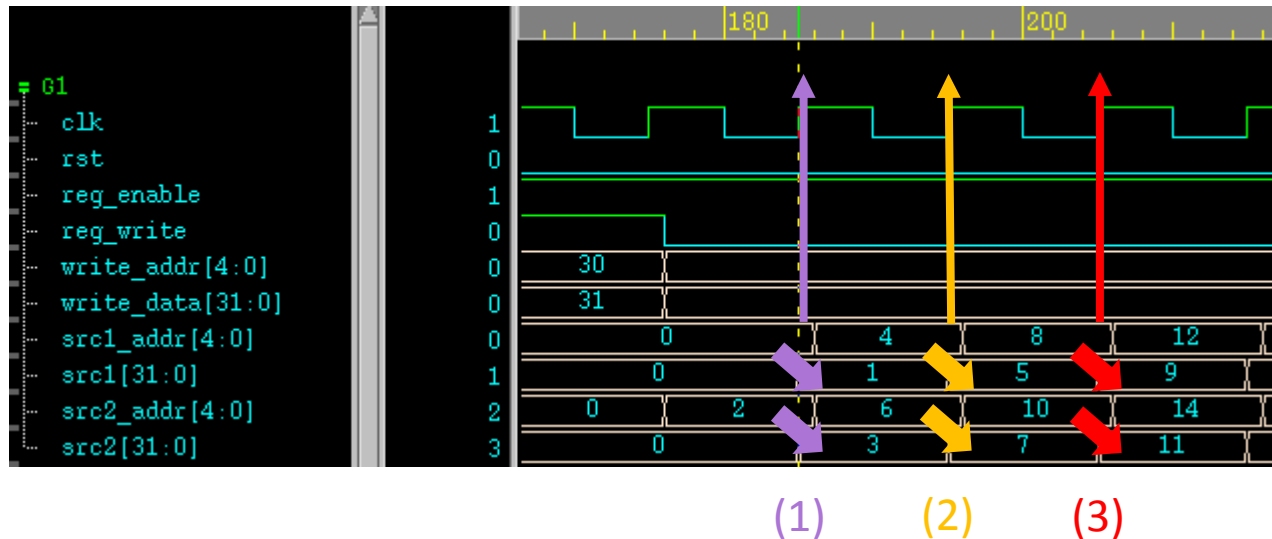

(1) clock positive edge ↑, register file is enable and in read mode

↑ → src1 = REG [0] = 32'd1, src2 = REG [2] = 32'd3

(2) clock positive edge ↑, register file is enable and in read mode

↑ → src1 = REG [4] = 32'd5, src2 = REG [6] = 32'd7

(3) clock positive edge ↑, register file is enable and in read mode


↑ → src1 = REG [8] = 32'd9, src2 = REG [10] = 32'd11

Lab B : Reference Code (1/2)


```

1  `timescale 1ns/10ps
2
3  // ----- define ----- //
4  `define DataSize    32
5  `define RegSize     32
6  `define AddrSize    5
7
8  module regfile (clk, rst, reg_enable, reg_write, src1_addr, src2_addr,
9                 write_addr, write_data, src1, src2);
10
11  // ----- input ----- //
12  input          clk;
13  input          rst;
14  input          reg_enable;
15  input          reg_write;
16  input  [`AddrSize-1:0] src1_addr;
17  input  [`AddrSize-1:0] src2_addr;
18  input  [`AddrSize-1:0] write_addr;
19  input  [`DataSize-1:0] write_data;
20
21  // ----- output ----- //
22  output  [`DataSize-1:0] src1;
23  output  [`DataSize-1:0] src2;
24
25  // ----- reg ----- //
26  reg  [`DataSize-1:0] src1;
27  reg  [`DataSize-1:0] src2;
28  reg  [`DataSize-1:0] REG [`RegSize-1:0];
29
30  integer i;

```

 

Lab B : Reference Code (2/2)

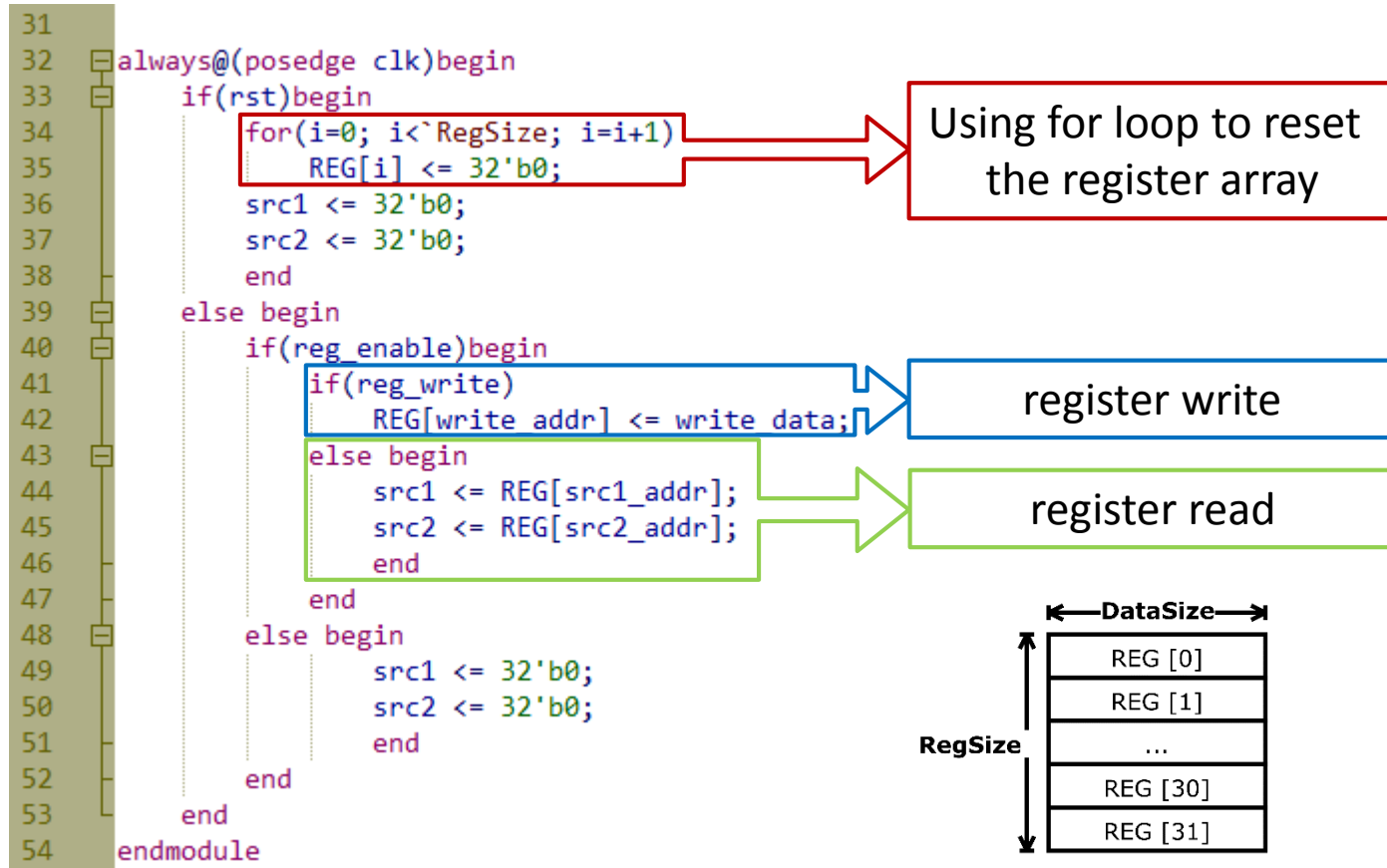

Lab C : Serial-In Parallel-Out Register File

- A special design of register file which use only **one** address to get **more than one** data in a register file simultaneously.
- Take a serial-in parallel-out 32 X 32 register file as an example:
 - ➔ It only has one read address port but **three** output ports.


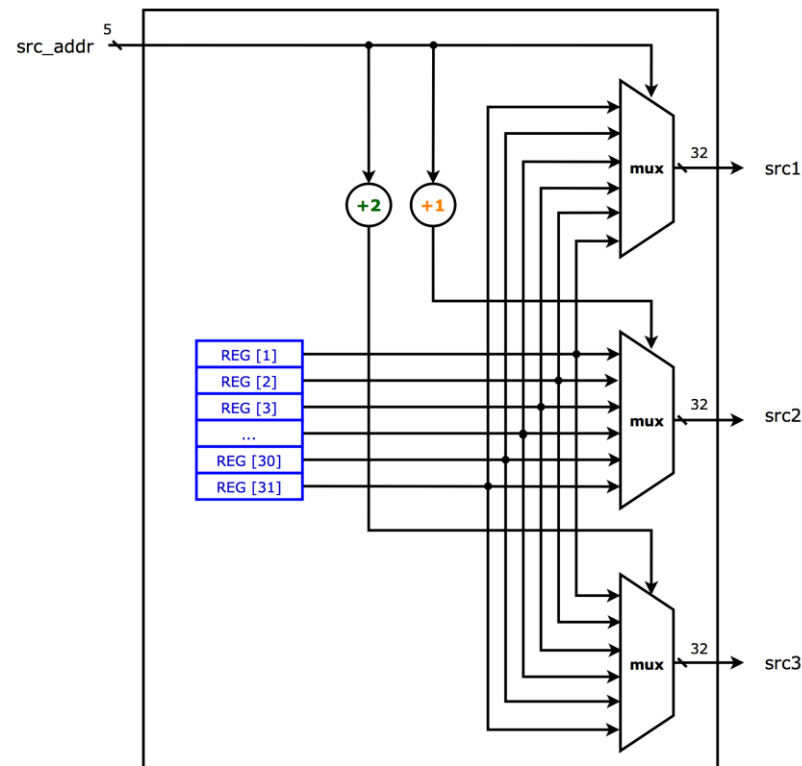


Fig. Read data from SIPO register file

Lab C : Serial-In Parallel-Out Register File


Port List

Signal	Type	Bits	Description
clk	input	1	clock
rst	input	1	reset
reg_enable	input	1	register file enable
reg_write	input	1	0 → read 1 → write
src_addr	input	5	source address
write_addr	input	5	write address
write_data	input	32	write data
src1	output	32	read data source1
src2	output	32	read data source2
src3	output	32	read data source3

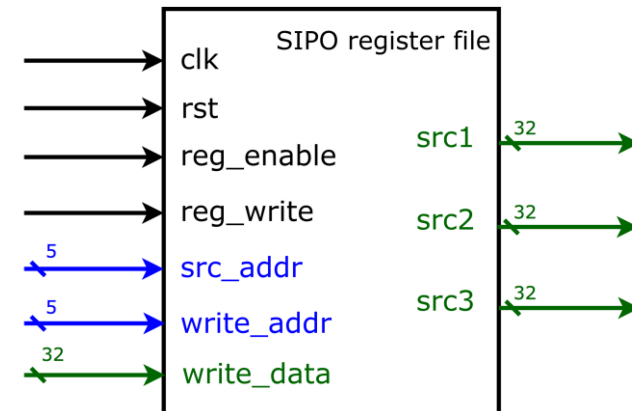

Lab C : Serial-In Parallel-Out Register File

□ How does it read?

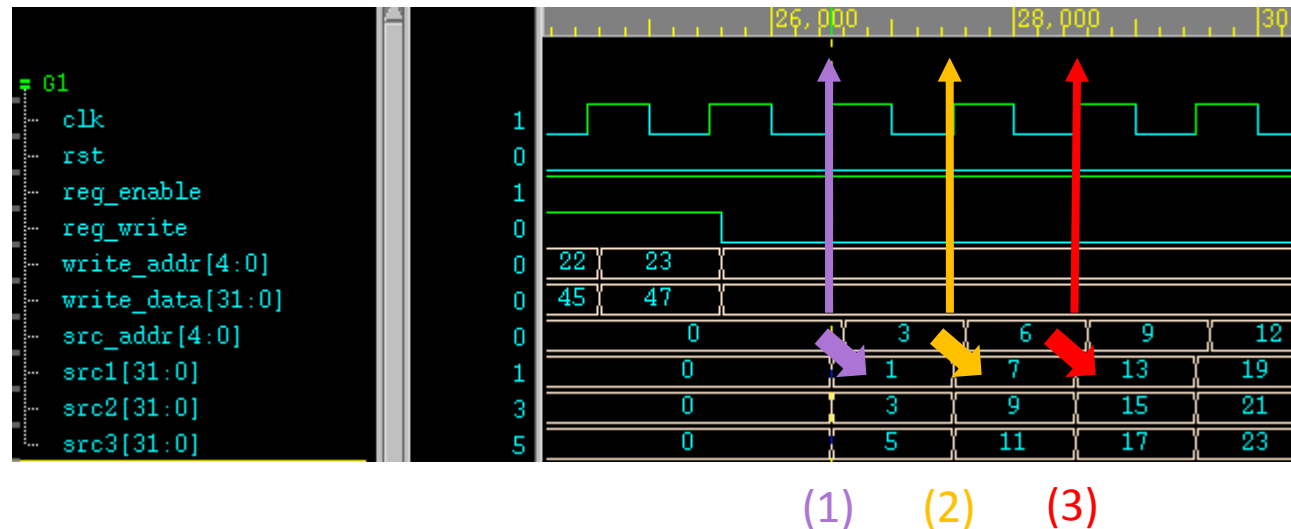

(1) clock positive edge ↑, register file is enable and in read mode

↑ → $\text{src1} = \text{REG}[0] = 32'd1$, $\text{src2} = \text{REG}[0+1] = 32'd3$, $\text{src3} = \text{REG}[0+2] = 32'd5$

(2) clock positive edge ↑, register file is enable and in read mode

↑ → $\text{src1} = \text{REG}[3] = 32'd7$, $\text{src2} = \text{REG}[3+1] = 32'd9$, $\text{src3} = \text{REG}[3+2] = 32'd11$

(3) clock positive edge ↑, register file is enable and in read mode

↑ → $\text{src1} = \text{REG}[6] = 32'd13$, $\text{src2} = \text{REG}[6+1] = 32'd15$, $\text{src3} = \text{REG}[6+2] = 32'd17$

Lab C : Reference Code (1/2)

```

1  `timescale 1ns/10ps
2
3  // ----- define ----- //
4  `define DataSize    32
5  `define RegSize     32
6  `define AddrSize    5
7
8  module regfile_sipo (clk, rst, reg_enable, reg_write, src_addr, write_addr,
9  | write_data, src1, src2, src3);
10 |
11 | // ----- input ----- //
12 | input          clk;
13 | input          rst;
14 | input          reg_enable;
15 | input          reg_write;
16 | input  [`AddrSize-1:0] src_addr;
17 | input  [`AddrSize-1:0] write_addr;
18 | input  [`DataSize-1:0] write_data;
19 |
20 | // ----- output ----- //
21 | output  [`DataSize-1:0] src1;
22 | output  [`DataSize-1:0] src2;
23 | output  [`DataSize-1:0] src3;
24 |
25 | // ----- reg ----- //
26 | reg  [`DataSize-1:0] src1;
27 | reg  [`DataSize-1:0] src2;
28 | reg  [`DataSize-1:0] src3;
29 | reg  [`DataSize-1:0] REG [`RegSize-1:0];
30 |
31 | integer i;

```


Lab C : Reference Code (1/3)

```

32
33 always@(posedge clk)begin
34     if(rst)begin
35         for(i=0; i<`RegSize; i=i+1)
36             REG[i] <= 32'b0;
37         src1 <= 32'b0;
38         src2 <= 32'b0;
39         src3 <= 32'b0;
40     end
41     else begin
42         if(reg_enable)begin
43             if(reg_write)
44                 REG[write_addr] <= write_data;
45             else begin
46                 src1 <= REG[src_addr];
47                 src2 <= REG[src_addr+1];
48                 src3 <= REG[src_addr+2];
49             end
50         end
51         else begin
52             src1 <= 32'b0;
53             src2 <= 32'b0;
54             src3 <= 32'b0;
55         end
56     end
57 end
58 endmodule


```

Diagram illustrating the register read operation:

register read

Lab D : Register File + ALU

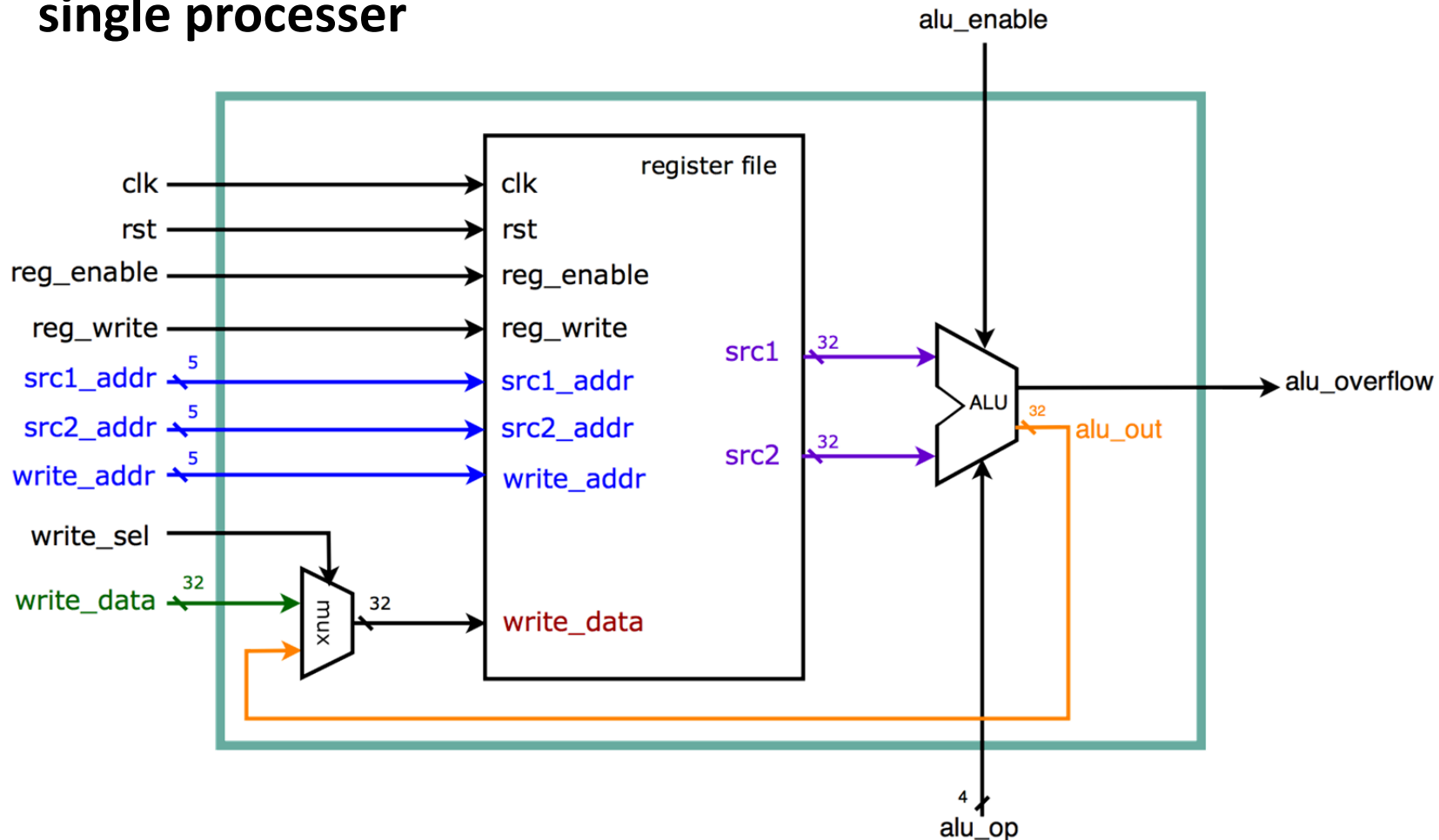- Combining a **32 x 32 Register File** and an **ALU** to form a subsystem that could carry out the basic operation of a single processor



Lab D : Register File + ALU


□ Port List

Signal	Type	Bits	Description
clk	input	1	clock
rst	input	1	reset
reg_enable	input	1	register file enable
reg_write	input	1	0 → read 1 → write
src1_addr	input	5	source1 address
src2_addr	input	5	source2 address
write_addr	input	5	write address
write_data	input	32	write data
alu_enable	input	1	0 → close 1 → open
alu_op	input	4	ALU operation code
write_sel	input	1	0 → write_data 1 → alu_out
alu_overflow	output	1	0 → no overflow 1 → overflow

Lab D : Register File + ALU

□ How does it work ?


➔ Write data into register file

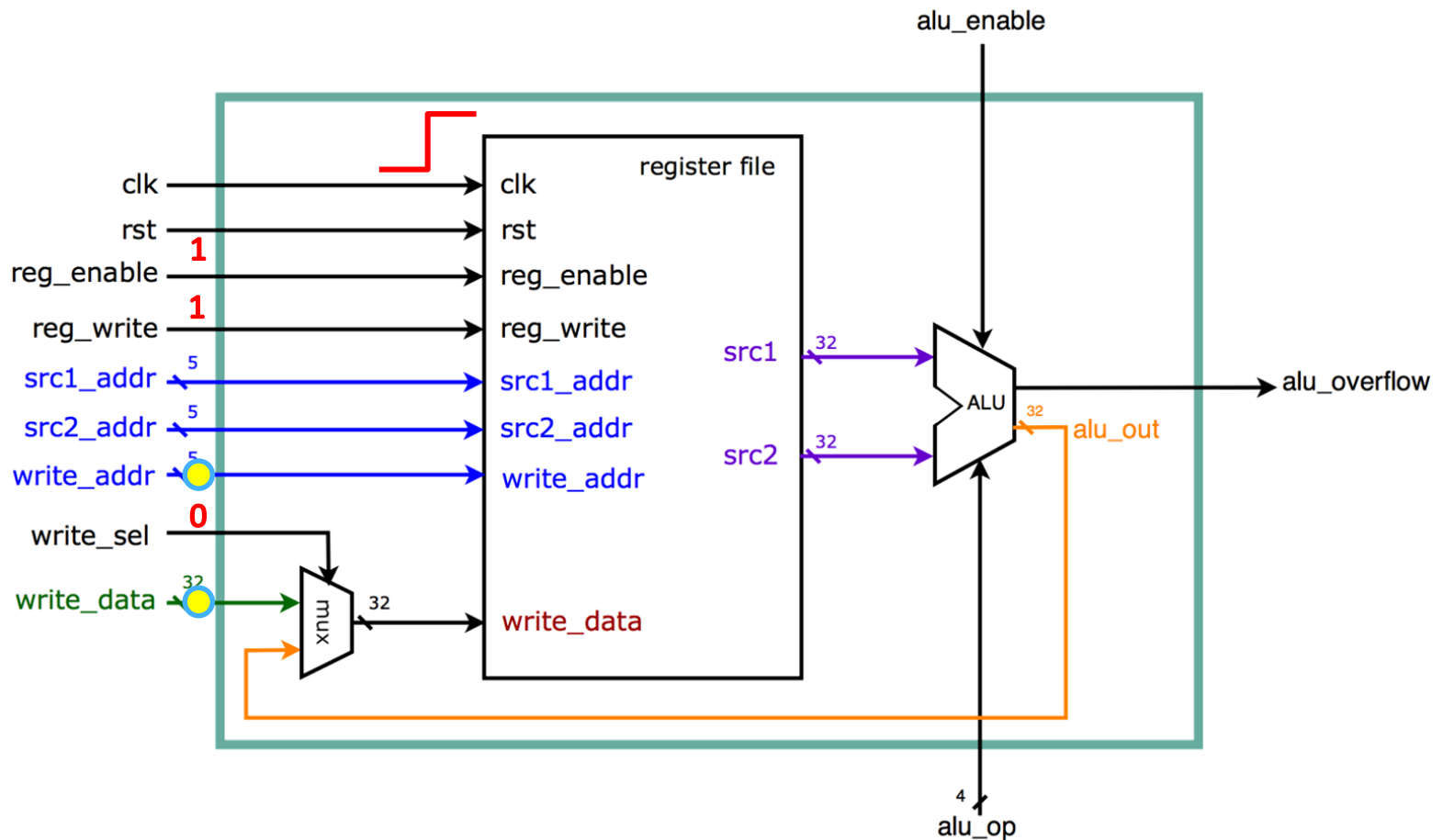

Lab D : Register File + ALU

□ How does it work ?


➔ Write data into register file

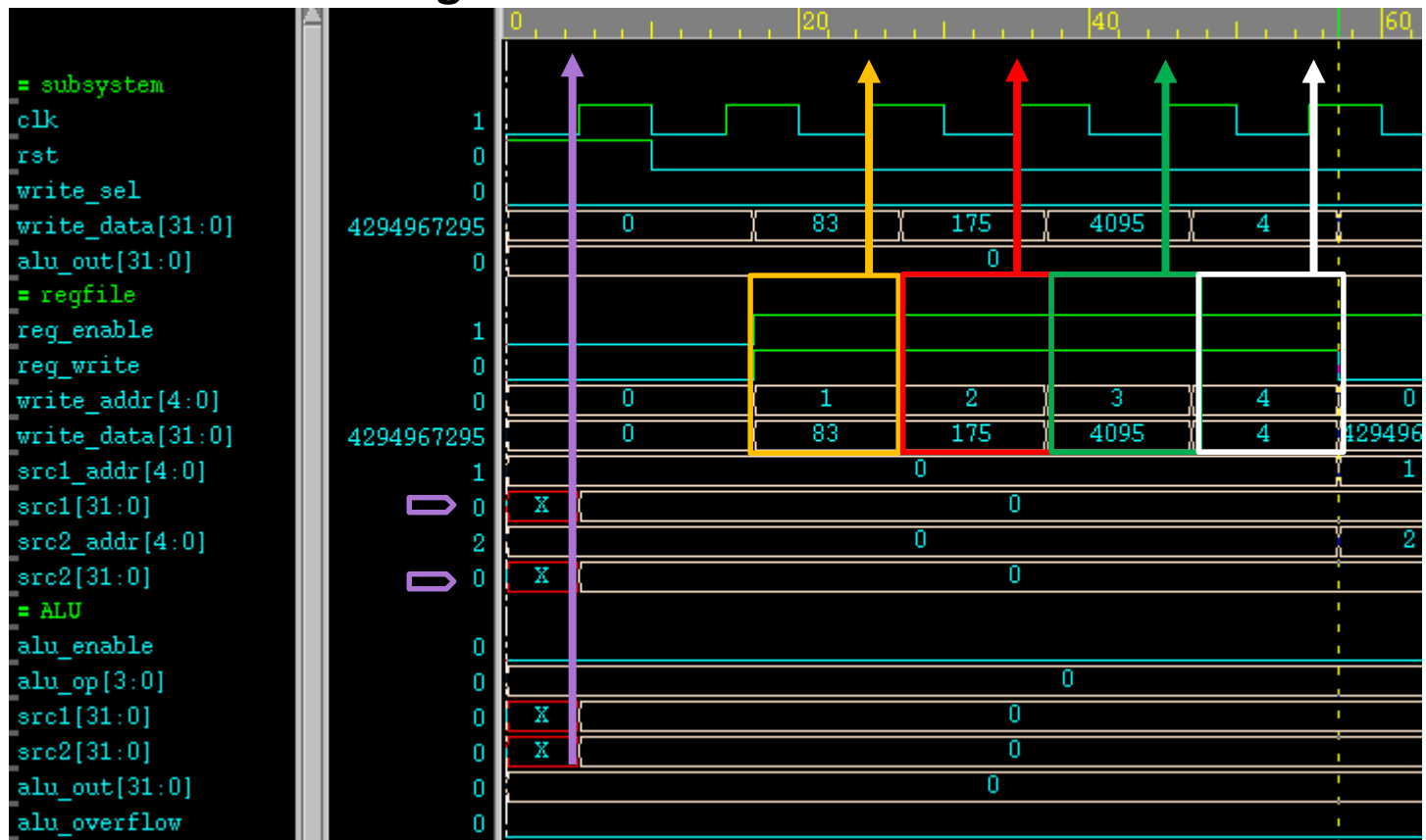

Lab D : Register File + ALU


□ How does it work ?

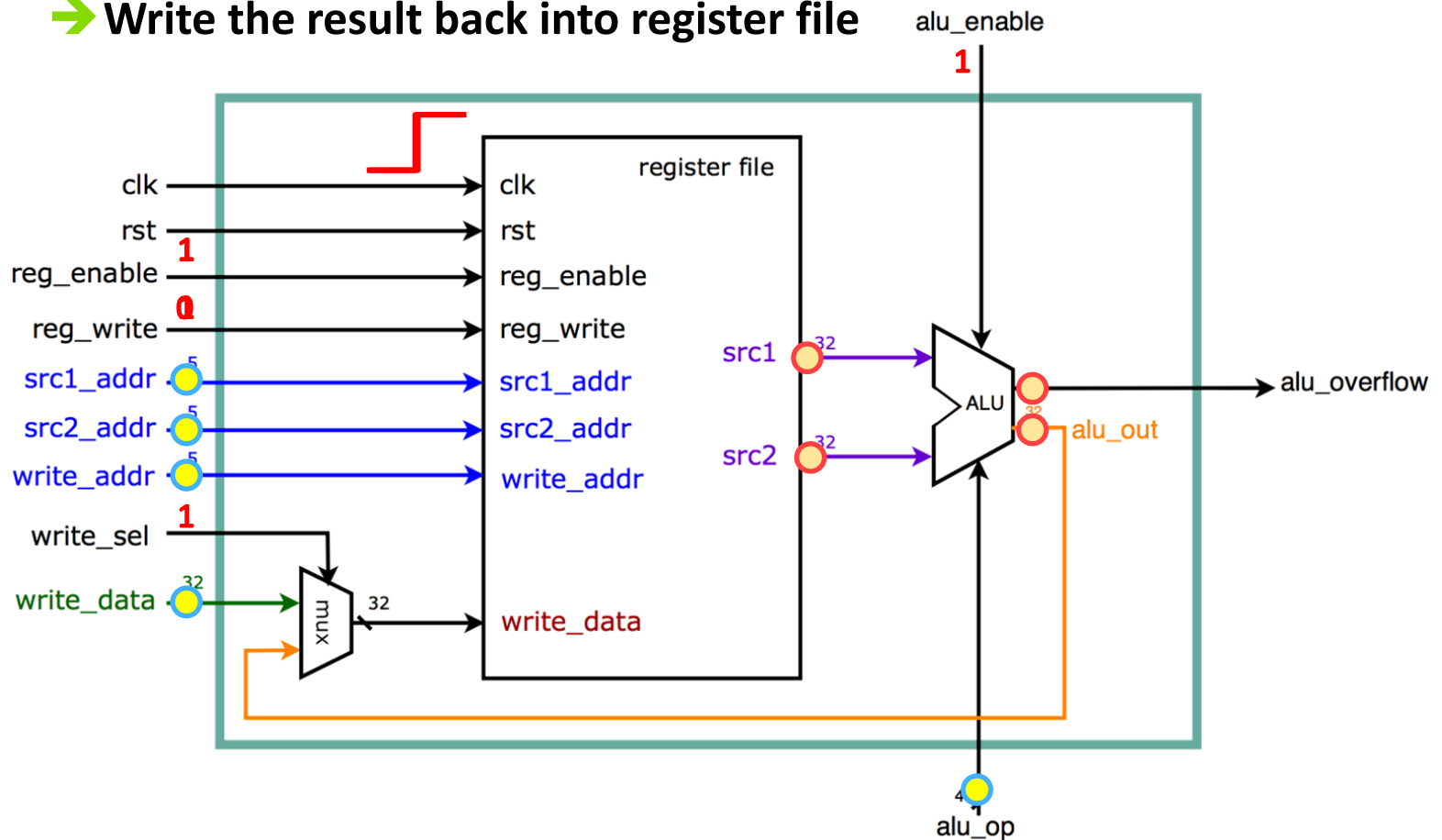- ➔ Read data from register file and execute by ALU
- ➔ Write the result back into register file



Lab D : Register File + ALU

□ How does it work ?

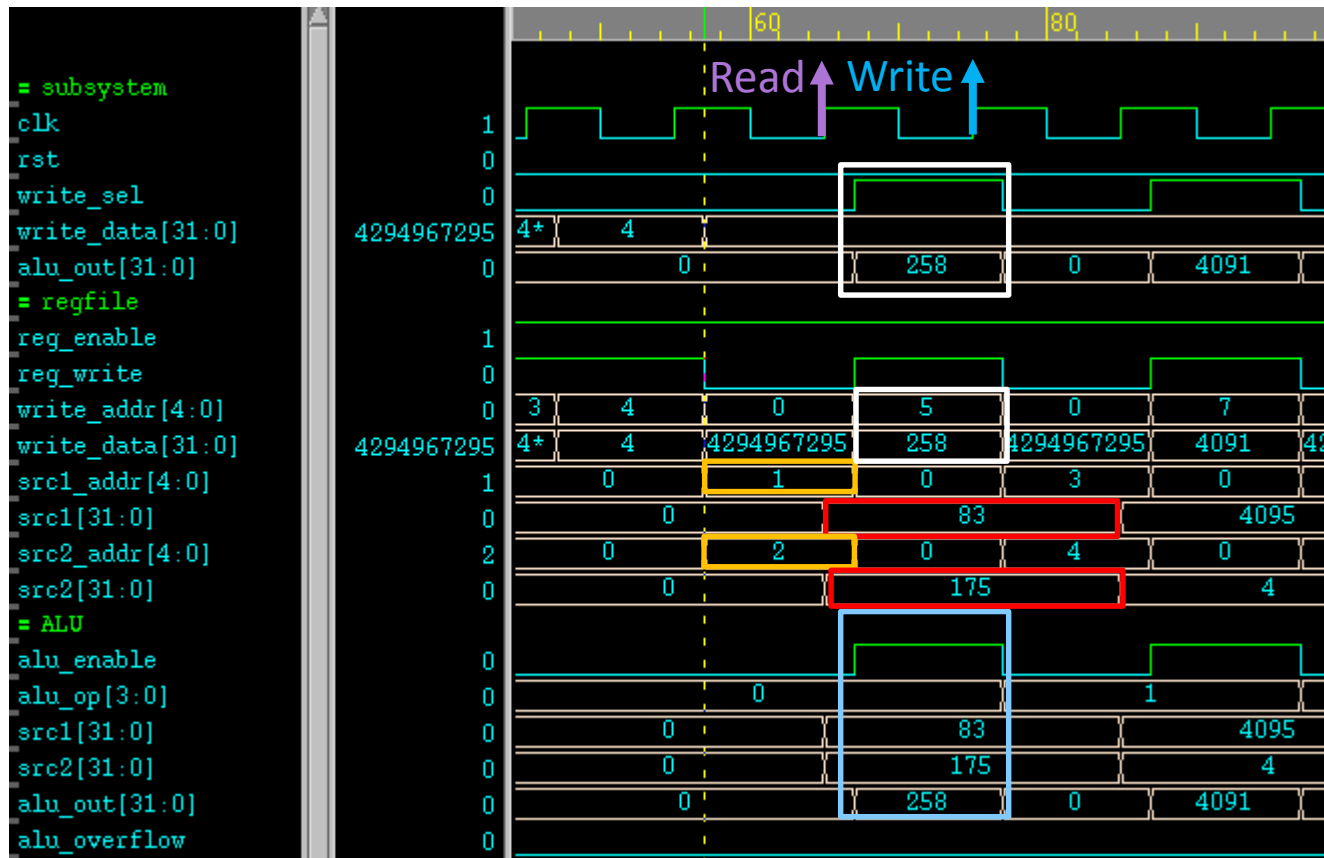

Lab5 Homework

□ ProbA

→ Implement another **8** instructions based on the ALU in LabA.

□ ProbB

→ Design a **64 X 32** register file based on LabB's structure.

□ ProbC

→ Design a **128 X 32** SIPO-register file based on LabC's structure with **5** output ports.

□ ProbD

→ Implement the subsystem in LabD using the components your designed in ProbA and ProbB.

Attention :

1. Make sure all your verilog code can be compiled in SOC lab.
2. Behavioral descriptions are acceptable.

Copy Reference code

□ Steps :

- Open the terminal command-line interface.
- Login the workstations. (**ssh -X vlsicad5(9))**
- % **cp -r /home/user2/vlsi16/vlsi1680/lab5 .**

01~15:vlsicad5

16~30:vlsicad9

Point